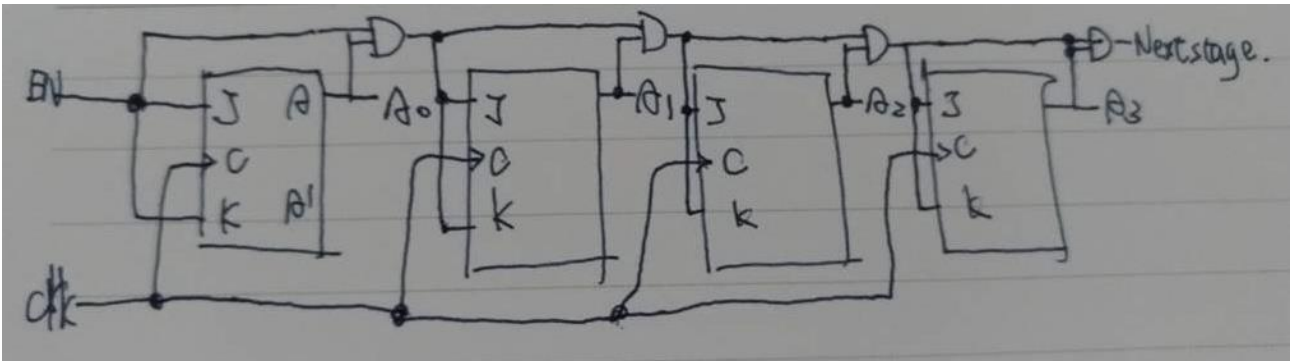



Pre-labs:

1. 4-bit synchronous binary up counter:

1.1 Logic diagram:



1.2 Verilog representation:

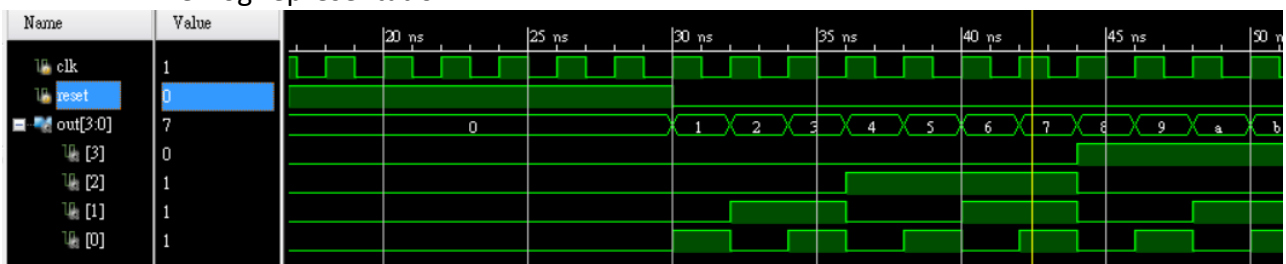

Verilog codes:

Module:

```

module lab03pre(
    input clk, input reset,
    output [3:0]out
);
    reg [3:0]out;

    always @(posedge clk or negedge reset)
        if(reset)
            out <= 4'd0;
        else
            out = out + 1;
endmodule

```

out++ when reset!=1,
out=0 when reset = 1

Testbench:

```

module lab03pre_t;

    reg clk; reg reset;
    wire [3:0] out;

    lab03pre uut(.clk(clk), .reset(reset), .out(out));

    initial begin
        clk = 1; reset = 0;
        #10 reset = 1;
        #20 reset = 0;
    end
    always
        #1 clk = ~clk;
endmodule


```

Experiments:

1. Frequency divider:

1.1 specification: a circuit that takes an input signal of a frequency f , and generates an output signal of a frequency $f_{out} = f/n$, where n is an integer. The n is 2^{27} in this case.

1.2 Block diagram:

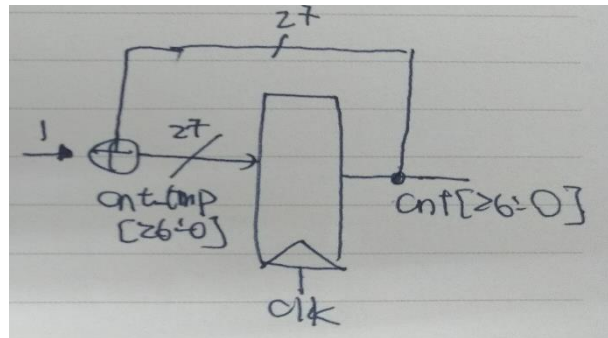

1.3 Implementation:

```
`define FREQ_DIV_BIT 27
module lab031(clk_out, clk, rst);
output clk_out;
input clk;
input rst;
reg[`FREQ_DIV_BIT-1:0] cnt;
reg[`FREQ_DIV_BIT-1:0] cnt_tmp;
wire clk_out;

assign clk_out= cnt[`FREQ_DIV_BIT-1];

always @(cnt)
cnt_tmp= cnt+ 1'b1;

always @(posedge clk or posedge rst)
if (rst)
cnt<= `FREQ_DIV_BIT'd0;
else
cnt<=cnt_tmp;
endmodule
```

One output signal(clk_out)

Input clock and reset(clk, rst)

a parameter [26:0]cnt to count to 2^{27}

temp parameter



the output signal is the 26th bit of "count"

count keeps ++

if reset == 1, count returns to 0

else count ++


FPGA:

  

2. Count-for-50M frequency divider:

2.1 Specification: a circuit that takes an input signal of a frequency f , and generates an output signal of a frequency: $f_{out} = f/n$, where n is an integer. The n is 50M in this case.

2.2 Block diagram:

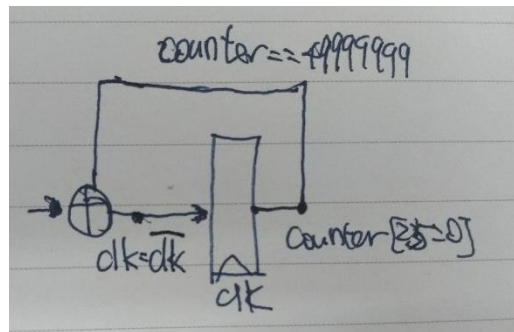

2.3 Implementation:

```
module lab032(clk,rst,clk_out);
input clk,rst;
output clk_out;
reg [25:0]counter;
reg clk_out;
```

Counter counts to 2^{26} ($67108864 > 50000000$)

```
always @(posedge clk or negedge rst)
```

```
begin
```

```
if(rst)
```

```
begin
```

```
    counter<=26'd0;
```

```
    clk_out <= 0;
```

```
end
```

```
else
```

```
begin
```

```
    if(counter==26'd49999999)
```

```
    begin
```

```
        counter<=26'd0;
```

```
        clk_out<=~clk_out;
```

```
    end
```

```
end
```

```
counter<=counter+1;
```

```
end
```

```
endmodule
```



If reset == 1, then counter returns to 0.

If counter counts to 49999999 (from 0)

Counter returns to 0.

$clk_out = \sim clk_out$

counter ++ (always)

  

3. 4-bit synchronous binary up counter:

```
module lab033(  
    input clk,  
    input rst,  
    output [3:0]b  
);
```

input clock and reset
output a 4-bit b

```
    reg [26:0]counter;  
    reg [3:0]b;
```

create a 27-bit counter

```
always @(posedge clk or negedge rst)  
begin  
    if(rst)  
    begin  
        counter<=27'd0;  
        b <= 4'd0;  
    end  
    else  
    begin  
        if(counter==27'd49999999)  
        begin  
            counter<=27'd0;  
            b <= b + 4'd1;  
        end  
        end  
        counter<=counter+1;  
    end  
endmodule
```

if reset is 1



counter return to 0
b return to 0

if reset is 0

if counter added to 49999999
counter return to 0
b ++

counter ++ (if reset == 0)

FPGA:

  

4. Single digit BCD up counter display on seven-segment display

```

`define SS_0 8'b00000011
`define SS_1 8'b10011111
`define SS_2 8'b00100101
`define SS_3 8'b00001101
`define SS_4 8'b10011001
`define SS_5 8'b01001001
`define SS_6 8'b01000001
`define SS_7 8'b00011111
`define SS_8 8'b00000001
`define SS_9 8'b00001001

```

Seven-segment display code

```

end
else
begin
if(counter==27'd49999999)
begin
counter<=27'd0;
b <= b + 4'd1;
if(b==4'd9)
begin
b <= 4'd0;
end
end
end
end
counter<=counter+1;

```

If counter == 49999999

(f = 50M)

Counter return to 0

b++

if b == 9

b return to 0

```

module lab034(
input clk,
input rst,
output [7:0]D_ssd
);

```

An output for 7-seg display

```

reg [26:0]counter;
reg [7:0]D_ssd;
reg [3:0]b;

```

A Counter to count to

49999999

b to calculate 1~10

```

always @(posedge clk or negedge rst)

```

```

begin

```

```

if(rst)

```

```

begin

```

if rst == 1 then return to 0

```

counter<=27'd0;

```

```

b <= 4'd0;

```

```

case (b)
4'd0: D_ssd = `SS_0;
4'd1: D_ssd = `SS_1;
4'd2: D_ssd = `SS_2;
4'd3: D_ssd = `SS_3;
4'd4: D_ssd = `SS_4;
4'd5: D_ssd = `SS_5;
4'd6: D_ssd = `SS_6;
4'd7: D_ssd = `SS_7;
4'd8: D_ssd = `SS_8;
4'd9: D_ssd = `SS_9;
default: D_ssd = 8'b01110001;
endcase
end
endmodule

```

counter ++

b turn to 7-seg display




Display module:

```

module lab034_ssd(
input clk,
input rst,
output [7:0]D_ssd,
output [3:0]ssd_ctl
);
lab034 U0(.clk(clk), .D_ssd(D_ssd), .rst(rst));
assign ssd_ctl = 4'b1110;
endmodule

```

FPGA:

   

Bonus: 30-second count-down timer:

```

`define SS_0 8'b00000011
`define SS_1 8'b10011111
`define SS_2 8'b00100101
`define SS_3 8'b00001101
`define SS_4 8'b10011001
`define SS_5 8'b01001001
`define SS_6 8'b01000001
`define SS_7 8'b00011111
`define SS_8 8'b00000001
`define SS_9 8'b00001001

module lab03bo(
    input clk,
    input rst,
    output [7:0]D_ssd,
    output [3:0]ssd_ctl
);
    reg [26:0]count;
    reg [7:0]D_ssd;
    reg [3:0]watch0;
    reg [3:0]watch1;
    reg [3:0]watch;
    reg [3:0]ssd_ctl;

    always @(posedge clk or negedge rst)
    begin
        if(rst)
        begin
            count <= 27'd0;
            watch0 <= 4'd0;
            watch1 <= 4'd3;
        end
        else
        begin
            if(count == 27'd49999999)
            begin
                count <= 27'd0;
                watch0 <= watch0 - 'd1;
                if(watch0 == 4'd0)
                begin
                    if(watch1 == 4'd0)
                    begin
                        watch0 <= 4'd0;
                        watch1 <= 4'd0;
                    end
                    else
                    begin
                        watch0 <= 4'd9;
                        watch1 <= watch1 - 4'd1;
                    end
                end
            end
            count <= count + 27'd1;
            case(count[17:16])
                2'b00 : ssd_ctl = 4'b1110;
                2'b01 : ssd_ctl = 4'b1101;
                2'b10 : ssd_ctl = 4'b1110;
                2'b11 : ssd_ctl = 4'b1101;
            endcase
            case(ssd_ctl)
                4'b1110: watch = watch0;
                4'b1101: watch = watch1;
            endcase
            case (watch)
                4'd0: D_ssd = `SS_0;
                4'd1: D_ssd = `SS_1;
                4'd2: D_ssd = `SS_2;
                4'd3: D_ssd = `SS_3;
                4'd4: D_ssd = `SS_4;
                4'd5: D_ssd = `SS_5;
                4'd6: D_ssd = `SS_6;
                4'd7: D_ssd = `SS_7;
                4'd8: D_ssd = `SS_8;
                4'd9: D_ssd = `SS_9;
                default: D_ssd = 8'b01110001;
            endcase
        end
    end
endmodule

```

Seven-segment display code

If rst == 1

return to 30

If count to 49999999

Count return to 0

Watch0 – 1 (first digit)

If watch0 == 0

Then watch1 – 1 (second digit)

and watch0 return to 9

If all == 0 (00)

Then stops at 00

An output for 7-seg display

An output for 7-seg control

A Counter to count to 49999999

Watch0 is the first digit

Watch1 is the second digit

Count continue ++

Give ssd_ctl a case of [17:16]

Then repeatedly change the on position on

7-seg display

Display the number on the right position

